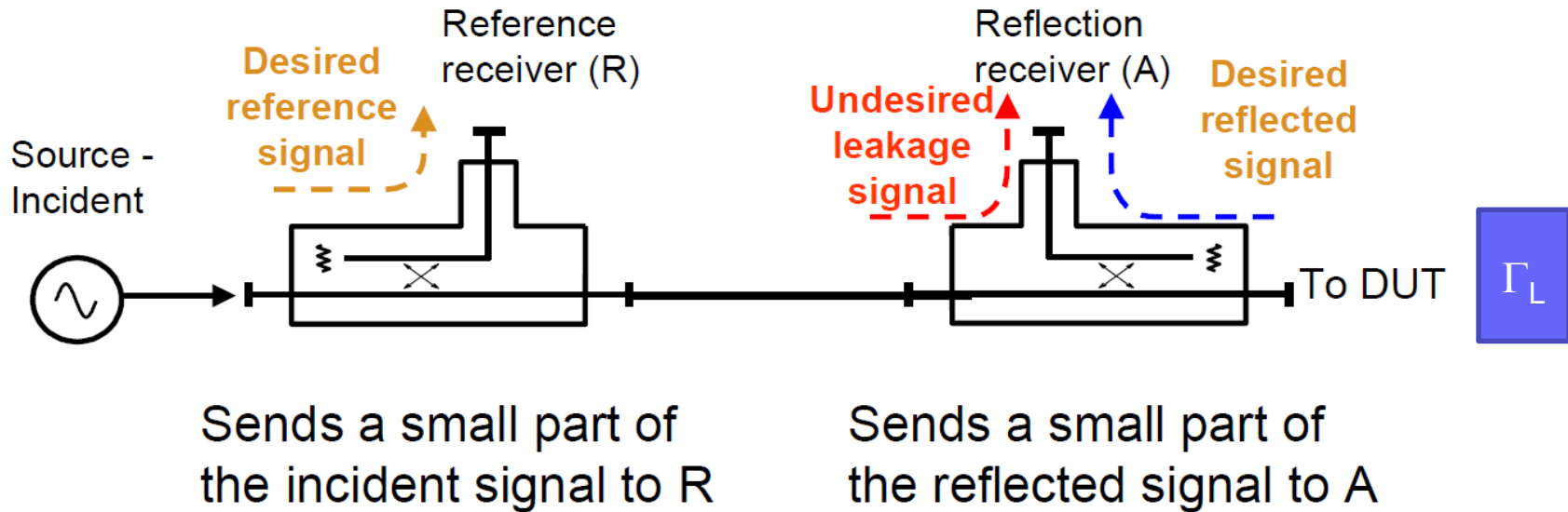


Radiofrequency Measurements


Reflection Measurements

4-port Reflectometer

A reflectometer is a circuit for measuring the reflection coefficient of a load, in amplitude and phase.



4-port Reflectometer

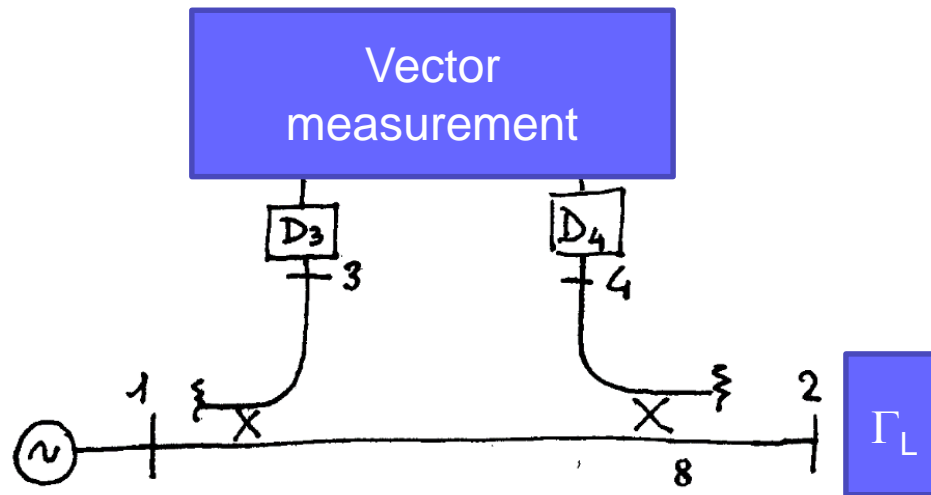

Ideal case:

- Infinite directivity ($S_{14} = S_{23} = 0$)
- Perfect matching of the couplers ($S_{kk} = 0$ $k = 1, \dots, 4$)
- Perfect matching of the detectors ($\Gamma_3 = \Gamma_4 = 0$)

Reflectometer: ideal case

$$b_3 = S_{31} a_1 = (S_{31} / S_{21}) b_2$$

$$b_4 = S_{42} a_2$$

$$b_4 / b_3 = v_4 / v_3 = (S_{42} S_{21} / S_{31}) \Gamma_L$$




$$\Gamma_L = C v_4 / v_3$$

C to be determined

There is need for 1 single measurement with a known load, for example a short circuit phase sensitive detection ($\Gamma_L = -1$)_{s.c.}


$$C = -(v_3 / v_4)_{s.c.}$$

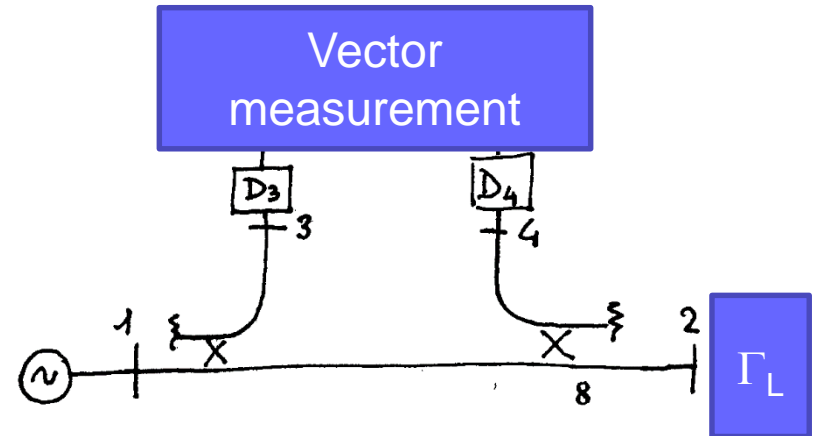v_3 and v_4 measured by a phase sensitive detection, after heterodyne conversion



Reflectometer: real case

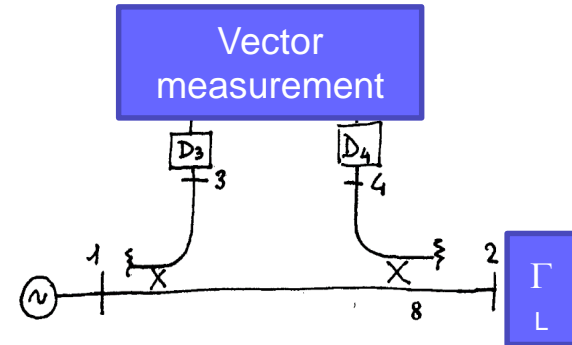After substitution of the last two equations we get 6 unknowns ($a_1, a_2, b_1, b_2, b_3, b_4$) and 4 equations. Supposing that the determinant of the new system is $\neq 0$ (it depends on the reflectometer structure), again, by substitutions we get 4 unknowns and 2 equations (always linear)



$$b_3 = \alpha_3 a_2 + \beta_3 b_2 = (\alpha_3 \Gamma_{l2} + \beta_3) b_2 \quad \Gamma_{l2} = a_2/b_2$$

$$b_4 = \alpha_4 a_2 + \beta_4 b_2 = (\alpha_4 \Gamma_{l2} + \beta_4) b_2$$

(structure close to be ideal $\iff |\alpha_3| \ll |\beta_3| \text{ e } |\alpha_4| \gg |\beta_4|$)

$$v_3 = \sqrt{Z_0} (a_3 + b_3) = \sqrt{Z_0} (\Gamma_3 + 1) b_3 = \sqrt{Z_0} (\Gamma_3 + 1) (\alpha_3 \Gamma_{l2} + \beta_3) b_2$$


$$v_4 = \sqrt{Z_0} (a_4 + b_4) = \sqrt{Z_0} (\Gamma_4 + 1) b_4 = \sqrt{Z_0} (\Gamma_4 + 1) (\alpha_4 \Gamma_{l2} + \beta_4) b_2$$



$$v_4/v_3 = [(\Gamma_4 + 1)/(\Gamma_3 + 1)] (\alpha_4 \Gamma_{l2} + \beta_4) / (\alpha_3 \Gamma_{l2} + \beta_3) = A (\Gamma_{l2} + B) / (\Gamma_{l2} + C)$$

Reflectometer: real case
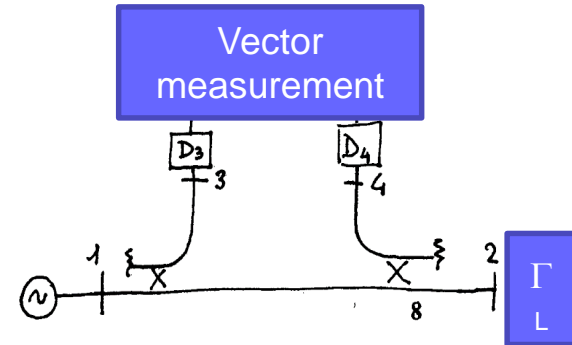
$$v_4/v_3 = A (\Gamma_{l_2} + B) / (\Gamma_{l_2} + C)$$



Even if the detectors have a different attenuation (and frequency response), the equation is still valid: there are **3 parameters to be determined**.

Standard procedure:

Applying **3 known loads** (typically short-circuit, open-circuit and matched load) and calculate the 3 coefficient for each frequency.